

Lab 5: Counters and Clocks

Jason Zhang

February 12, 2023

1 Part I

1. Export the subcircuit schematic as an image and include it in your report.

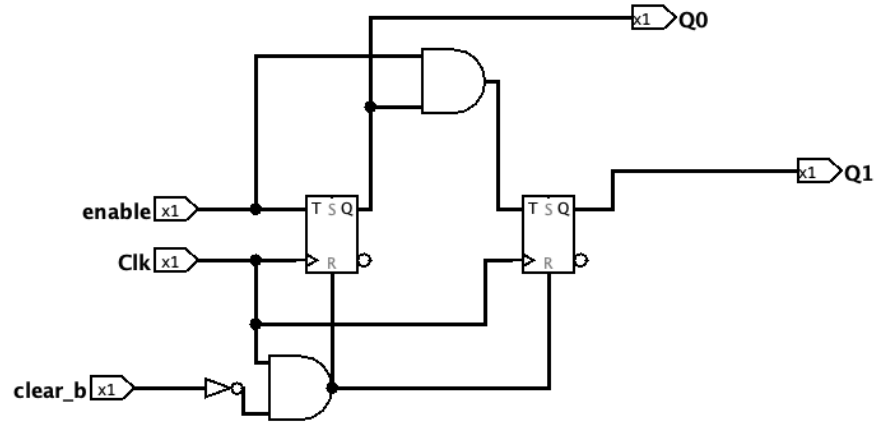


Figure 1: A schematic of counter2.

2. Export the subcircuit schematic as an image and include it in your report.

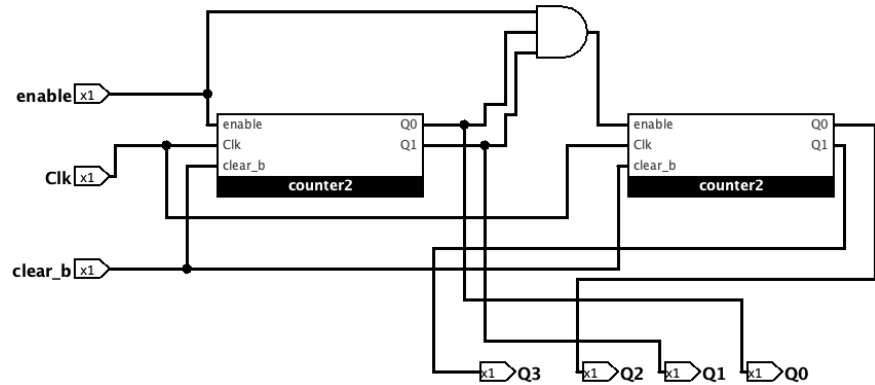


Figure 2: A schematic of counter4.

3. Export the timing diagram as an image and include it in your report.
4. Export the subcircuit schematic as an image and include it in your report.

2 Part II

1. Export the subcircuit schematic as an image and include it in your report.

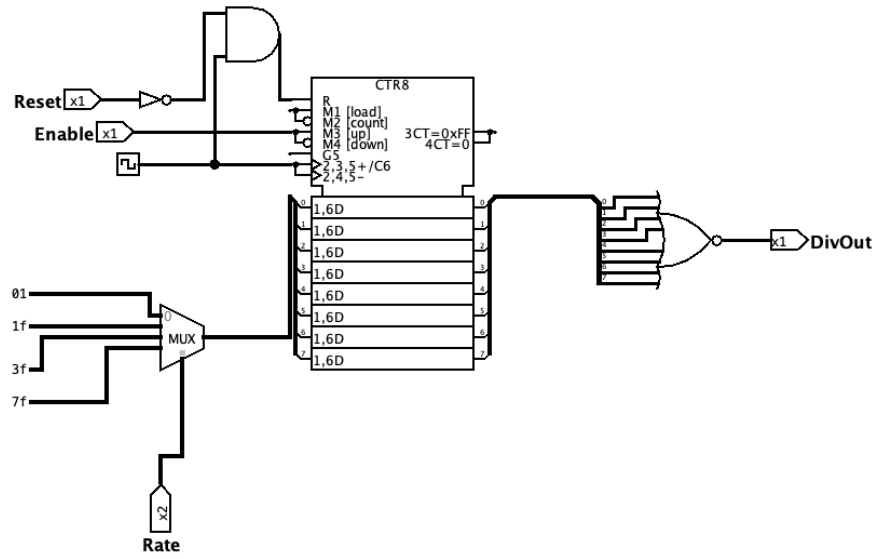


Figure 5: A schematic of rate_divider.

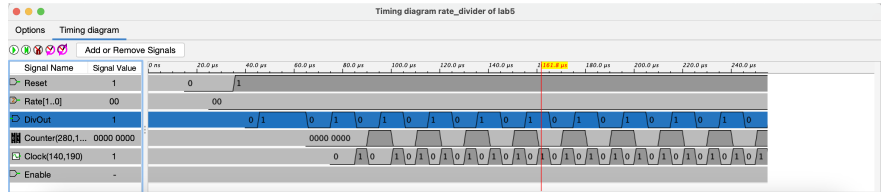


Figure 6: A timing simulation of rate_divider.

Letter	Morse Code	Pattern Representation (pattern length is <u>14</u> bits)
S	• • •	10101000000000
T	—	11100000000000
U	• • —	10101110000000
V	• • • —	10101011100000
W	• — —	10111011100000
X	— • • —	11101010111000
Y	— • — —	11101011101110
Z	— — • •	11101110101000

Table 1: Morse Pattern Representation with fixed bit-width

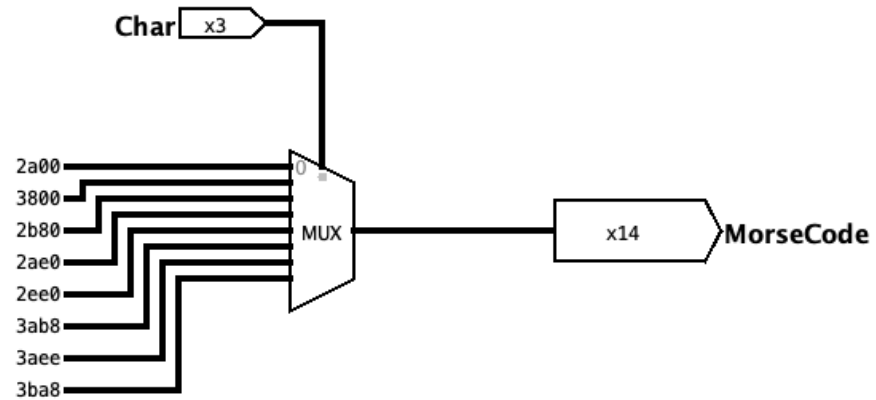


Figure 7: A schematic of MORSE.LUT.